



Technician License Course

Chapter 3.2

Electricity, Components and Circuits

Lesson Plan Module 6

Larry Hall
KD0RIU

Electronics – Controlling the Flow of Current

- To make an electronic device (like a radio) do something useful (like a receiver), we need to **control and manipulate the flow of current**.
- There are a number of different electronic components that we use to do this.

The Resistor

- The function of the **resistor is to restrict (limit) the flow of current** through it.


- Circuit Symbol



The Capacitor

- The function of the **capacitor is to temporarily store electric field or charge.**
 - Like a very temporary storage battery.
 - Stores energy in an electrostatic field of electrons.

- Circuit Symbol

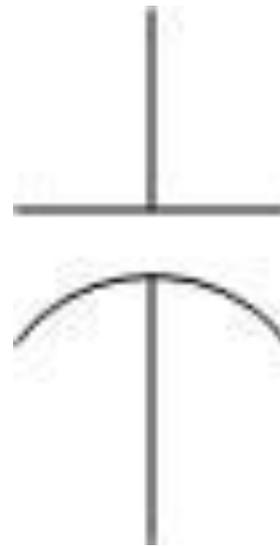

The Inductor

- The function of the **inductor is to temporarily store energy in a magnetic field** around the inductor.
 - Is basically a coil of wire.

- Circuit Symbol



Resonance

- Because capacitors and inductors store energy in different ways, **the stored energy can actually cancel each other under the right conditions.**
 - Capacitors – electric field
 - Inductors – magnetic field
- Cancelled current = **no reactance**, just **leaving resistance.**

Resonant Antenna

- If an antenna is designed correctly, the **capacitive reactance cancels the inductive reactance.**
- Theoretically, the resulting **reactance is zero.**
 - Leaving only resistance – meaning minimum impediment to the radio frequency currents flowing in the antenna and sending the radio wave into space.


Antennas are Part Capacitor – Part Inductor – Part Resistor

- **Antennas actually have characteristics of capacitor, inductor and resistor electronic components.**
- Capacitors and inductors, because they store energy in fields, react differently to ac than dc.
 - Special kind of resistance to the flow of ac – called reactance.

The Transistor


- The function of the **transistor is to variably control the flow of current.**
 - Much like an **electronically controlled valve.**
 - An analogy, the faucet in your sink.

- Circuit Symbol

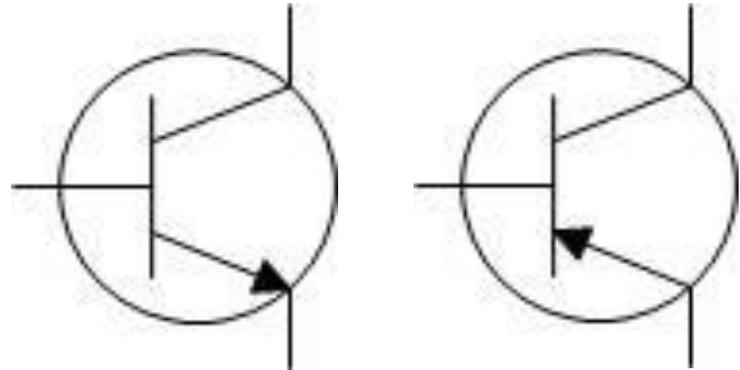

The Integrated Circuit

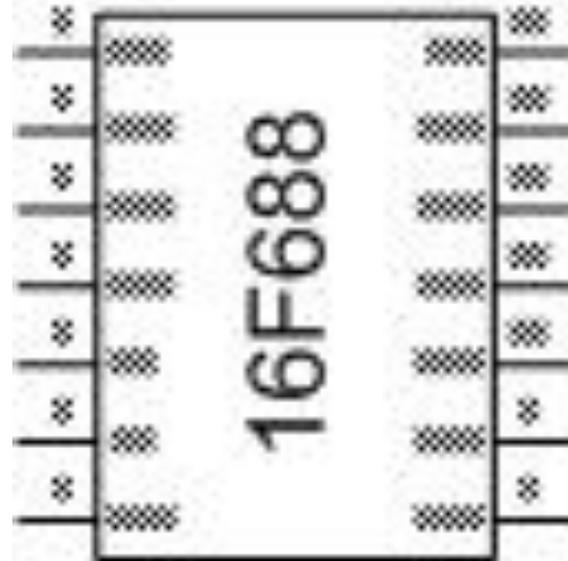- The **integrated circuit** is a collection of components contained in one device that accomplishes a specific task.
 - Acts like a “black-box”
- Circuit Symbol



Protective Components – Intentional Open Circuits

- **Fuses and circuit breakers are designed to interrupt the flow of current** if the current becomes uncontrolled.

- **Fuses blow** – one time protection.
- **Circuit breakers trip** – can be reset and reused.


- Circuit Symbol




Other Circuit Symbols

Schematic Symbols Used in Circuit Diagrams

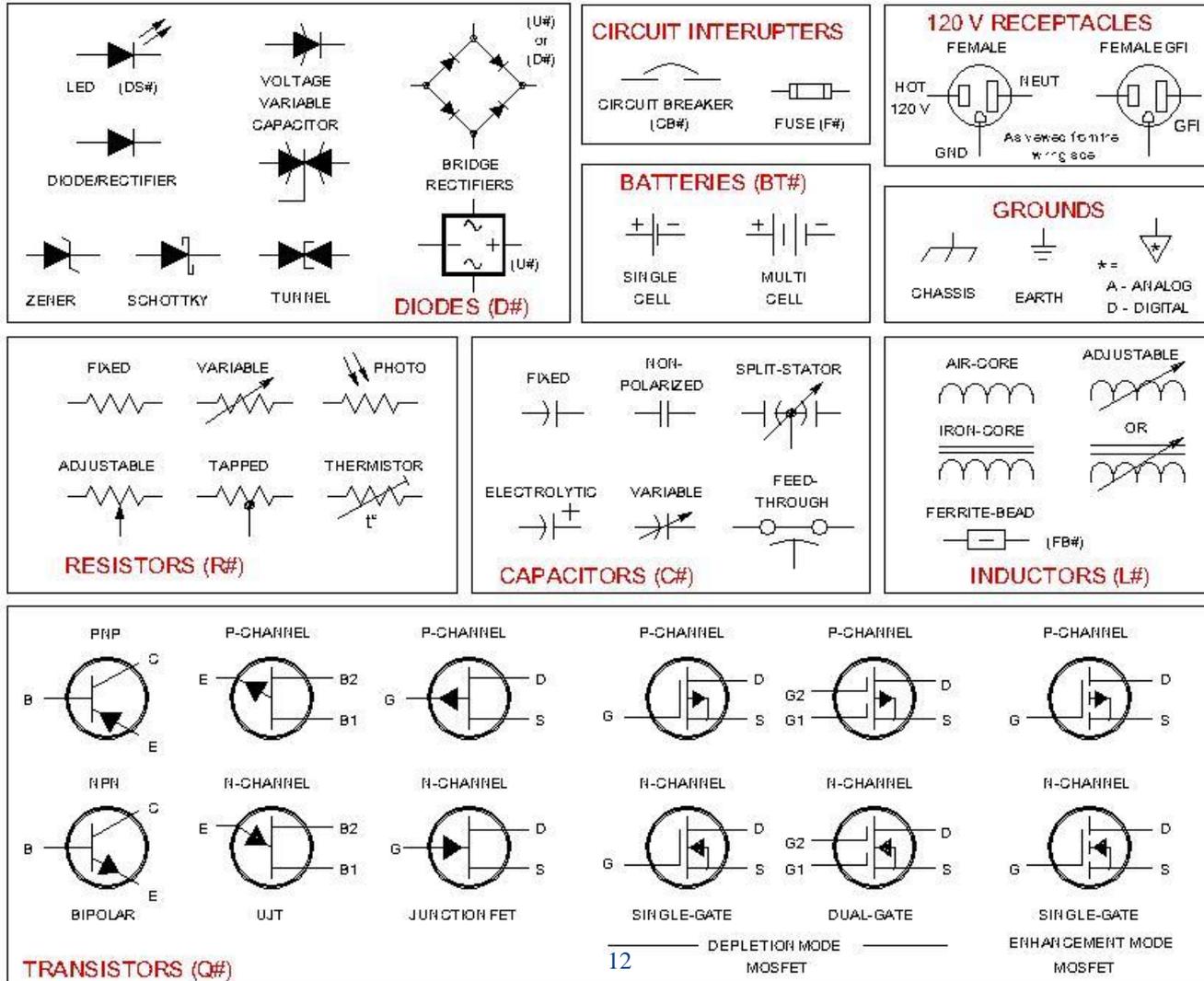Labelling conventions: # is a sequential number. (X#) is the component designator. Examples - C3, L11, R8, Q3



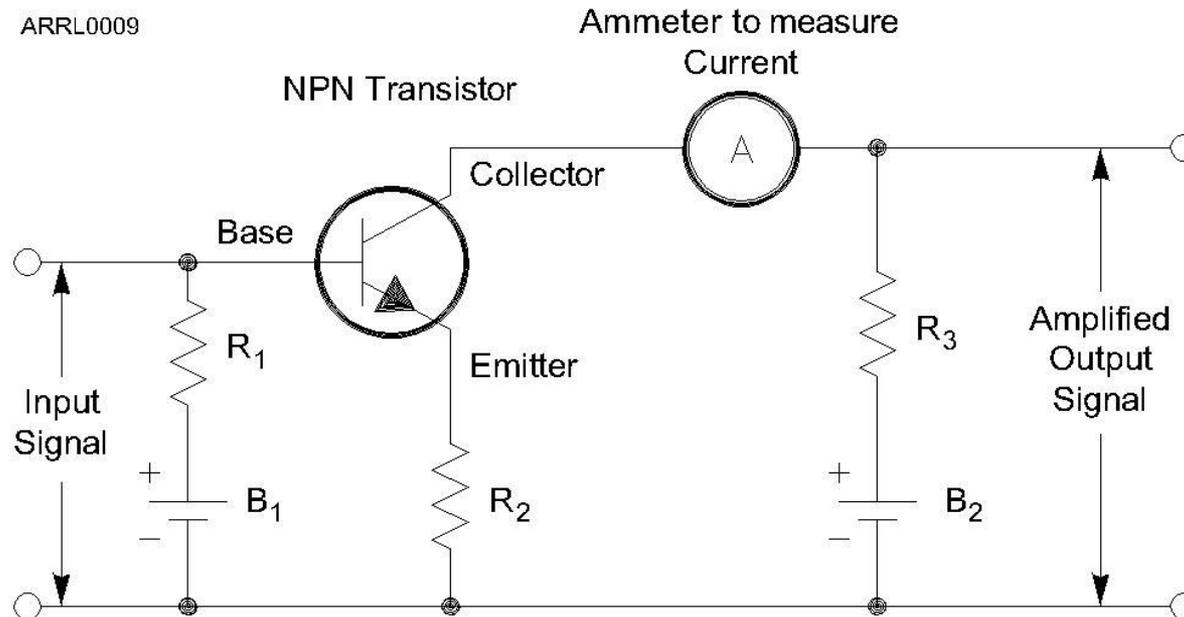Putting It All Together in a Circuit Diagram



What is the ability to store energy in an electric field called? (T5C01)

- * A. Inductance
- * B. Resistance
- * C. Tolerance
- * D. Capacitance

What is **the ability to store energy in an electric field** called? (T5C01)

- * A. Inductance
- * B. Resistance
- * C. Tolerance
- * **D. Capacitance**

What is the basic unit of capacitance? (T5C02)

- * A. The farad
- * B. The ohm
- * C. The volt
- * D. The henry

What is the basic **unit of capacitance**? (T5C02)

- * **A. The farad**
- * B. The ohm
- * C. The volt
- * D. The henry

What is the ability to store energy in a magnetic field called? (T5C03)

- * A. Admittance
- * B. Capacitance
- * C. Resistance
- * D. Inductance

What is the ability to store energy in a magnetic field called? (T5C03)

- * A. Admittance
- * B. Capacitance
- * C. Resistance
- * **D. Inductance**

What is the basic unit of inductance? (T5C04)

- * A. The coulomb
- * B. The farad
- * C. The henry
- * D. The ohm

What is the basic **unit of inductance**? (T5C04)

- * A. The coulomb
- * B. The farad
- * **C. The henry**
- * D. The ohm

What electrical component is used to oppose the flow of current in a DC circuit? (T6A01)

- * A. Inductor
- * B. Resistor
- * C. Voltmeter
- * D. Transformer

What **electrical component** is used to **oppose** the flow of current in a DC circuit? (T6A01)

- * A. Inductor
- * **B. Resistor**
- * C. Voltmeter
- * D. Transformer

What type of component is often used as an adjustable volume control? (T6A02)

- * A. Fixed resistor
- * B. Power resistor
- * C. Potentiometer
- * D. Transformer

What type of **component** is often **used as an adjustable volume control?** (T6A02)

- * A. Fixed resistor
- * B. Power resistor
- * **C. Potentiometer**
- * D. Transformer

What electrical parameter is controlled by a potentiometer? (T6A03)

- * A. Inductance
- * B. Resistance
- * C. Capacitance
- * D. Field strength

What electrical parameter is controlled by a potentiometer? (T6A03)

- * A. Inductance
- * **B. Resistance**
- * C. Capacitance
- * D. Field strength

What electrical component stores energy in an electric field? (T6A04)

- * A. Resistor
- * B. Capacitor
- * C. Inductor
- * D. Diode

What **electrical component stores energy in an electric field?** (T6A04)

- * A. Resistor
- * **B. Capacitor**
- * C. Inductor
- * D. Diode

What type of electrical component consists of two or more conductive surfaces separated by an insulator? (T6A05)

- * A. Resistor
- * B. Potentiometer
- * C. Oscillator
- * D. Capacitor

What type of electrical component consists of two or more conductive surfaces separated by an insulator? (T6A05)

- * A. Resistor
- * B. Potentiometer
- * C. Oscillator
- * **D. Capacitor**

What type of electrical component stores energy in a magnetic field? (T6A06)

- * A. Resistor
- * B. Capacitor
- * C. Inductor
- * D. Diode

What type of **electrical component stores energy in a magnetic field?** (T6A06)

- * A. Resistor
- * B. Capacitor
- * **C. Inductor**
- * D. Diode

What electrical component is usually composed of a coil of wire? (T6A07)

- * A. Switch
- * B. Capacitor
- * C. Diode
- * D. Inductor

What electrical component is usually **composed of a coil of wire?** (T6A07)

- * A. Switch
- * B. Capacitor
- * C. Diode
- * **D. Inductor**

What electrical component is used to connect or disconnect electrical circuits? (T6A08)

- * A. Zener diode
- * B. Switch
- * C. Inductor
- * D. Variable resistor

What electrical component is used to **connect or disconnect electrical circuits**? (T6A08)

- * A. Zener diode
- * **B. Switch**
- * C. Inductor
- * D. Variable resistor

What electrical component is used to protect other circuit components from current overloads? (T6A09)

- * A. Fuse
- * B. Capacitor
- * C. Shield
- * D. Inductor

What electrical component is used to protect other circuit components from current overloads? (T6A09)

- * **A. Fuse**
- * B. Capacitor
- * C. Shield
- * D. Inductor

What class of electronic components is capable of using a voltage or current signal to control current flow? (T6B01)

- * A. Capacitors
- * B. Inductors
- * C. Resistors
- * D. Transistors

What class of electronic components is capable of using a voltage or current signal to control current flow? (T6B01)

- * A. Capacitors
- * B. Inductors
- * C. Resistors
- * **D. Transistors**

What electronic component allows current to flow in only one direction? (T6B02)

- * A. Resistor
- * B. Fuse
- * C. Diode
- * D. Driven element

What electronic component allows current to flow in only one direction? (T6B02)

- * A. Resistor
- * B. Fuse
- * **C. Diode**
- * D. Driven element

Which of these components can be used as an electronic switch or amplifier? (T6B03)

- * A. Oscillator
- * B. Potentiometer
- * C. Transistor
- * D. Voltmeter

Which of these components can be used as an **electronic switch or amplifier**? (T6B03)

- * A. Oscillator
- * B. Potentiometer
- * **C. Transistor**
- * D. Voltmeter

Which of these components is made of three layers of semiconductor material? (T6B04)

- * A. Alternator
- * B. Bipolar junction transistor
- * C. Triode
- * D. Pentagrid converter

Which of these components is made of three layers of semiconductor material? (T6B04)

- * A. Alternator
- * **B. Bipolar junction transistor**
- * C. Triode
- * D. Pentagrid converter

Which of the following electronic components can amplify signals? (T6B05)

- * A. Transistor
- * B. Variable resistor
- * C. Electrolytic capacitor
- * D. Multi-cell battery

Which of the following electronic components can amplify signals? (T6B05)

- * **A. Transistor**
- * B. Variable resistor
- * C. Electrolytic capacitor
- * D. Multi-cell battery

How is a semiconductor diode's cathode lead usually identified? (T6B06)

- * A. With the word "cathode"
- * B. With a stripe
- * C. With the letter "C"
- * D. All of these choices are correct

How is a semiconductor diode's cathode lead usually identified? (T6B06)

- * A. With the word "cathode"
- * **B. With a stripe**
- * C. With the letter "C"
- * D. All of these choices are correct

What does the abbreviation “LED” stand for? (T6B07)

- * A. Low Emission Diode
- * B. Light Emitting Diode
- * C. Liquid Emission Detector
- * D. Long Echo Delay

What does the **abbreviation “LED”** stand for? (T6B07)

- * A. Low Emission Diode
- * **B. Light Emitting Diode**
- * C. Liquid Emission Detector
- * D. Long Echo Delay

What does the abbreviation “FET” stand for? (T6B08)

- * A. Field Effect Transistor
- * B. Fast Electron Transistor
- * C. Free Electron Transition
- * D. Field Emission Thickness

What does the **abbreviation “FET”** stand for? (T6B08)

- * **A. Field Effect Transistor**
- * B. Fast Electron Transistor
- * C. Free Electron Transition
- * D. Field Emission Thickness

What are the names of the two electrodes of a diode? (T6B09)

- * A. Plus and minus
- * B. Source and drain
- * C. Anode and cathode
- * D. Gate and base

What are the names of the two electrodes of a diode? (T6B09)

- * A. Plus and minus
- * B. Source and drain
- * **C. Anode and cathode**
- * D. Gate and base

Which semiconductor component has an emitter electrode? (T6B10)

- * A. Bipolar transistor
- * B. Field effect transistor
- * C. Silicon diode
- * D. Bridge rectifier

Which semiconductor component has an **emitter** electrode? (T6B10)

- * **A. Bipolar transistor**
- * B. Field effect transistor
- * C. Silicon diode
- * D. Bridge rectifier

Which semiconductor component has a gate electrode? (T6B11)

- * A. Bipolar transistor
- * B. Field effect transistor
- * C. Silicon diode
- * D. Bridge rectifier

Which semiconductor component has a **gate** electrode? (T6B11)

- * A. Bipolar transistor
- * **B. Field effect transistor**
- * C. Silicon diode
- * D. Bridge rectifier

What is the term that describes a transistor's ability to amplify a signal? (T6B12)

- * A. Gain
- * B. Forward resistance
- * C. Forward voltage drop
- * D. On resistance

What is the **term** that describes a **transistor's ability to amplify a signal**? (T6B12)

- * **A. Gain**
- * B. Forward resistance
- * C. Forward voltage drop
- * D. On resistance

What is the name for standardized representations of components in an electrical wiring diagram? (T6C01)

- * A. Electrical depictions
- * B. Grey sketch
- * C. Schematic symbols
- * D. Component callouts

What is the name for **standardized representations of components** in an electrical wiring diagram? (T6C01)

- * A. Electrical depictions
- * B. Grey sketch
- * **C. Schematic symbols**
- * D. Component callouts

Which of the following is accurately represented in electrical circuit schematic diagrams? (T6C13)

- * A. Wire lengths
- * B. Physical appearance of components
- * C. The way components are interconnected
- * D. All of these choices are correct

Which of the following is accurately represented in electrical circuit schematic diagrams? (T6C13)

- * A. Wire lengths
- * B. Physical appearance of components
- * **C. The way components are interconnected**
- * D. All of these choices are correct

Which of the following devices or circuits changes an alternating current into a varying direct current signal? (T6D01)

- * A. Transformer
- * B. Rectifier
- * C. Amplifier
- * D. Reflector

Which of the following devices or circuits changes an alternating current into a varying direct current signal? (T6D01)

- * A. Transformer
- * **B. Rectifier**
- * C. Amplifier
- * D. Reflector

Which best describes a relay? (T6D02)

- * A. A switch controlled by an electromagnet
- * B. A current controlled amplifier
- * C. An optical sensor
- * D. A pass transistor

Which best describes a **relay**? (T6D02)

- * **A. A switch controlled by an electromagnet**
- * B. A current controlled amplifier
- * C. An optical sensor
- * D. A pass transistor

Which of the following can be used to display signal strength on a numeric scale? (T6D04)

- * A. Potentiometer
- * B. Transistor
- * C. Meter
- * D. Relay

Which of the following can be used to **display signal strength on a numeric scale**? (T6D04)

- * A. Potentiometer
- * B. Transistor
- * **C. Meter**
- * D. Relay

What component is commonly used to change 120V AC house current to a lower AC voltage for other uses? (T6D06)

- * A. Variable capacitor
- * B. Transformer
- * C. Transistor
- * D. Diode

What component is commonly used to change 120V AC house current to a lower AC voltage for other uses? (T6D06)

- * A. Variable capacitor
- * **B. Transformer**
- * C. Transistor
- * D. Diode

Which of the following is commonly used as a visual indicator? (T6D07)

- * A. LED
- * B. FET
- * C. Zener diode
- * D. Bipolar transistor

Which of the following is commonly used as a **visual indicator**? (T6D07)

- * **A. LED**
- * B. FET
- * C. Zener diode
- * D. Bipolar transistor

Which of the following is used together with an inductor to make a tuned circuit? (T6D08)

- * A. Resistor
- * B. Zener diode
- * C. Potentiometer
- * D. Capacitor

Which of the following is **used together with an inductor to make a tuned circuit?** (T6D08)

- * A. Resistor
- * B. Zener diode
- * C. Potentiometer
- * **D. Capacitor**

What is the name of the device that combines several semiconductors and other components into one package? (T6D09)

- * A. Transducer
- * B. Multi-pole relay
- * C. Integrated circuit
- * D. Transformer

What is the name of the **device that combines several semiconductors and other components into one package?** (T6D09)

- * A. Transducer
- * B. Multi-pole relay
- * **C. Integrated circuit**
- * D. Transformer

What is the purpose of a fuse in an electrical circuit? (T0A04)

- * A. To prevent power supply ripple from damaging a circuit
- * B. To interrupt power in case of overload
- * C. To limit current to prevent shocks
- * D. All of these choices are correct

What is the **purpose of a fuse** in an electrical circuit? (T0A04)

- * A. To prevent power supply ripple from damaging a circuit
- * **B. To interrupt power in case of overload**
- * C. To limit current to prevent shocks
- * D. All of these choices are correct

Why is it unwise to install a 20-ampere fuse in the place of a 5 ampere fuse? (T0A05)

- * A. The larger fuse would be likely to blow because it is rated for higher current
- * B. The power supply ripple would greatly increase
- * C. Excessive current could cause a fire
- * D. All of these choices are correct

Why is it unwise to install a 20-ampere fuse in the place of a 5 ampere fuse? (T0A05)

- * A. The larger fuse would be likely to blow because it is rated for higher current
- * B. The power supply ripple would greatly increase
- * **C. Excessive current could cause a fire**
- * D. All of these choices are correct