

Welcome Back !!  
to  
Week # 5 of Class  
for  
EXTRA CLASS Radio License



# Chapter 6

## Radio Circuits and Systems

George McCarville  
WBØCNK

# Chapter 6

Pg: 6-1

- 6.1 - Amplifiers
- 6.2 - Signal Processing
- 6.3 - Digital Signal Processing (DSP)  
- Software Defined Radio (SDR)
- 6.4 - Filters and Impedance Matching
- 6.5 - Power Supplies (presented today)

## 6.5 Power Supplies

Pg: 6-42

# Power Supplies

## Linear Voltage Regulators

Pg: 6-42

# Introduction to Linear Voltage Regulators

The voltage of most simple power sources such as batteries or basic rectifier circuits, varies inversely with the load current.

- The more current the, more voltage drops.
- Voltage constantly varies as the device draws more or less power.

Why?

- Limited energy storage at the desired voltage.
- Lack of rapid energy conversion or storage at point of use.

A voltage regulation circuit

- Is usually included in most electronic devices to stabilize voltage and or current under changing load conditions.

## **Linear Voltage Regulators:**

Linear voltage regulators are one major category of voltage regulators.

In these circuits, regulation is accomplished by varying the conduction of a control element in the load current. The control element is varied to maintain the output voltage at a constant level.

- How does a linear electronic voltage regulator work?
  - The conduction of a control element is varied to maintain a constant output voltage.

# Power Supplies


## Linear Voltage Regulators

Pg: 6-42

# Introduction to Linear Voltage Regulators

- **Shunt Analog voltage regulator**

Because the Zener diode controls the output voltage by drawing current from the power source in parallel with the load, it is called a shunt regulator.

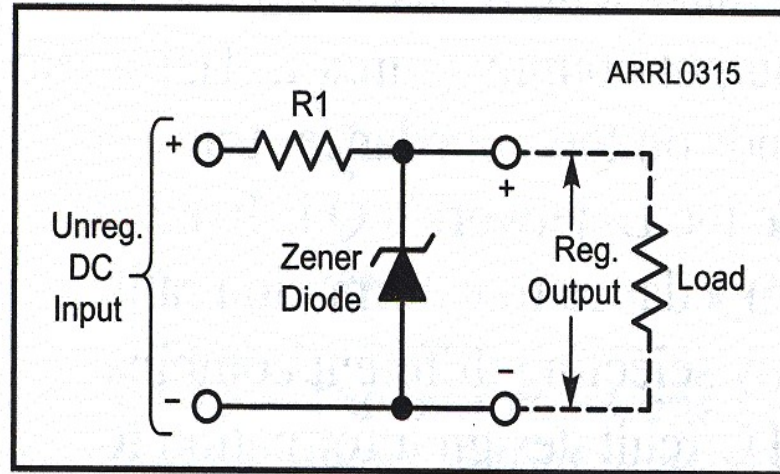

**Figure 6-45 — A Zener-diode voltage regulator circuit in which R1 is the control element.**

Recall:

Zener Diode:

- Conducts at its avalanche voltage
- A Large change in avalanche current results in only a small change in voltage across the zener.
- Available for various common voltages.

- E7D05 Which of the following types of linear voltage regulator operates by loading the unregulated voltage source?
  - A shunt regulator


# Power Supplies

## Linear Voltage Regulators
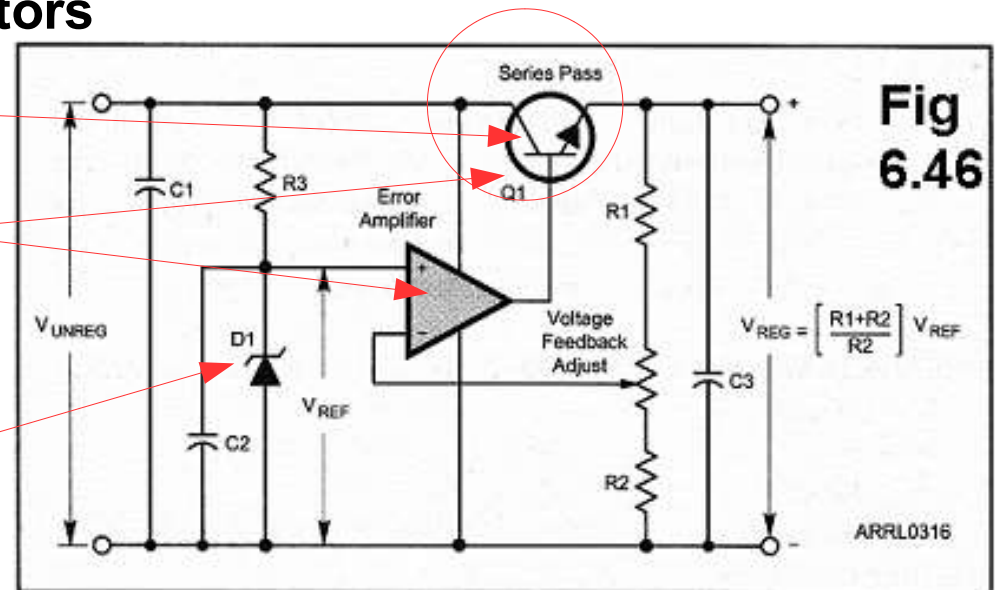
### Shunt and series Regulators

- **Linear Series Analog voltage regulators**

- Control Element is the BJT pass transistor (Q1).
- Base current controlled by the error amplifier.
- The OP Amp error amplifier compares a fraction of the output voltage to the Zener Diode voltage reference and adjusts the pass transistor base current until the output voltage has the correct value. Recall Op Amps



- E7D08 What type of circuit is shown in Figure 6.46?
  - ➔ Linear voltage regulator
- E7D03 What device is used as a stable voltage reference? ➔ A Zener diode
- E7D06 What is the purpose of Q1 in the circuit shown in Figure 6-46?
  - ➔ It controls the current to keep the output voltage constant

# Power Supplies


## Linear Voltage Regulators

### Shunt and series Regulation

Pg: 6-43

- **Linear Series Analog voltage regulators**

- **C1** serves to filter the unregulated input supply voltage.
- **C2** serves to bypass(route) hum, ripple and noise from the Zener output around the voltage reference.
- **R1 & R2 & Potentiometer** provide a sample of the output voltage and place a small load on the regulator.
- A series regulator requires a minimum level of voltage drop called the drop-out voltage across the pass element so that it can respond to changes in the load current and maintain constant output voltage
- **C3** across the output terminals prevent the regulator from oscillating if the load is removed or is very small.
- **E7D12** What is the dropout voltage of a linear voltage regulator?  
Minimum input-to-output voltage required to maintain regulation.
- **D07** What is the purpose of C2 in the circuit shown in Figure 6.46?  
→ It bypasses rectifier output ripple around D1

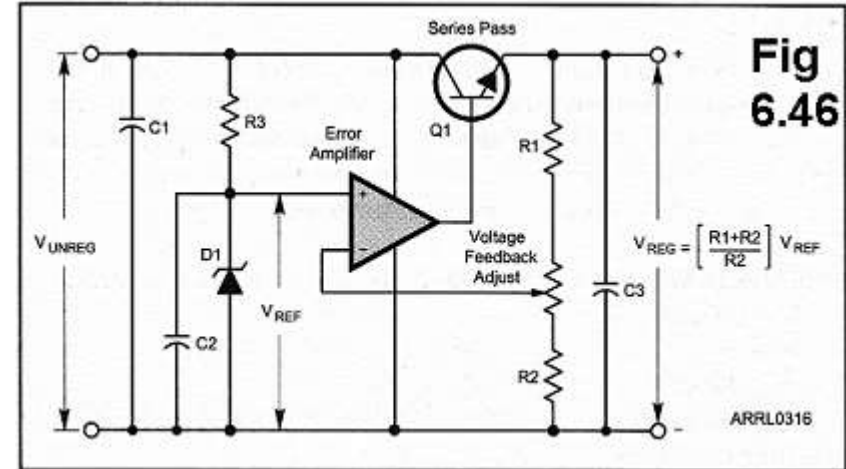

# Power Supplies

## Linear Voltage Regulators

### Efficiency & Power Dissipation

Pg: 6-44

#### Series and Shunt Regulators

- Both dissipate a lot of input power as heat to maintain constant voltage (Loss).

$$\text{Efficiency (in \%)} = 100\% \times \frac{\text{Power Out}}{\text{Power In}} \quad \text{Eq. 6.5}$$

$$P_{\text{DISS}} = (V_{\text{IN}} - V_{\text{OUT}}) \times I_{\text{OUT}} \quad \text{Eq. 6.6}$$

- E7D13** Which of the following calculates power dissipated by a series linear voltage regulator? **Voltage difference from input to output multiplied by output current**



- E7D04** Which of the following describes a three-terminal voltage regulator? **A series regulator**


## Battery Charging Regulators

1st of 2 categories of Special Voltage Regulators
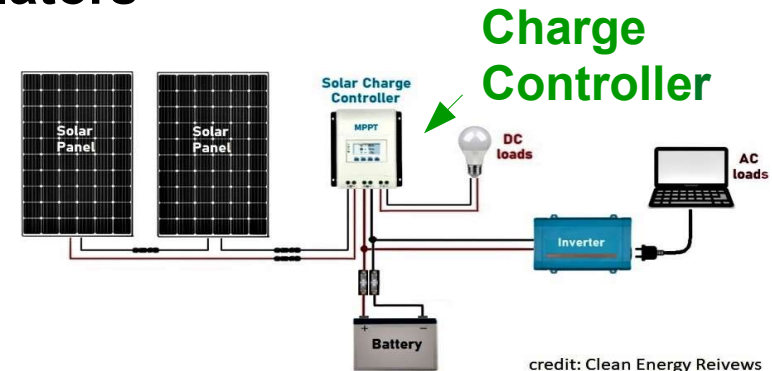
### Charge Controller:

Special voltage regulator for charging batteries.

- Are Important if using an intermittent power source like wind or solar panels etc.
- Applies current at the correct rate
  - Initially enough to reach correct voltage
  - Then just enough to maintain the optimum voltage
- Each different type of battery chemistry requires a different type of controller
  - Lead acid, Lithium, NiMH etc.
- How long will a fully charge battery will power your equipment?



**Battery Energy Rating amp-hours**  
————— = hours  
**Your Current Needs amps**

**Example:**  
 $\frac{150 \text{ Amp hours}}{12 \text{ Amps}} = 12.5 \text{ hours}$

- **E7D09 How is battery operating time calculated?**  
→ **Capacity in amp-hours divided by average current**

## Switching Regulators

### 2nd of Two categories of Special Voltage Regulators

#### **Switching Regulator:**

- Supplies equipment with DC power.
- The Control Voltage is switched **entirely ON** or **entirely OFF**
- Usually done with a BJT or MOSFET.
- Highly efficient, but poor designs can cause RF interference.
  
- The switching circuit stores energy in the magnetic field of inductors or transformers, then releases it to an output filter.
  
- Duty Cycle of the control element controls the rate energy is stored & released and is automatically adjusted for the correct output voltage.
  
- Switching frequencies – Are usually in the tens of Kilohertz
  - This reduces physical sizes needed of transformers, inductors & capacitors.
- **E7D02 How does a switchmode voltage regulator work?**
  - ➔ **By varying the duty cycle of pulses input to a filter**

## Switching Regulators

**E7D10 Why is a switching type power supply less expensive and lighter than an equivalent linear power supply?**

→ **The high frequency inverter design uses much smaller transformers and filter components for an equivalent power output**

**E4E12 What causes interference received as a series of carriers at regular intervals across a wide frequency range?**

→ **Switch-mode power supplies.**

# Power Supplies

## High Voltage Techniques

### Capacitors

Pg: 6-45

#### High Voltage Power Supplies

- Have unique construction requirements.
- Circuits require special physical spacing between leads & components to prevent arcing.
- At turn on: A step-start [relay] charges the capacitors gradually -then fully This is to limit inrush current through rectifier diodes etc.
- Capacitors connected in series require resistors across them to:
  - equalizing voltages across the caps,
  - provide a minimum load,
  - serve as bleeder resistors to discharge the caps when power is off.
- Safety cautions: Lethal voltages
- **E7D14**      Older oil filled capacitors may contain PCBs(cancer).

**What is the purpose of connecting equal-value resistors across power supply filter capacitors connected in series? → All of these are correct:**

- A. Equalize the voltage across each capacitor**
- B. Discharge the capacitors when voltage is removed**
- C. Provide a minimum load on the supply**
- D. All these choices are correct**

# Power Supplies

## High Voltage Techniques

### Capacitors

Pg: 6-45

## High Voltage Power Supplies



High Voltage  
Power Transformer

High Voltage  
Capacitors

Power conditioning  
board with **Step Start**.

**E7D15 What is the purpose of a step-start circuit in a high-voltage power supply? → To allow the filter capacitors to charge gradually**

END

END

Credits:  
ARRL: materials used with permission / [www.arrl.org/copyright](http://www.arrl.org/copyright)  
Wikipedia & internet: images & .GIF